


Example 1. Rotation of 8-bit vector using CASE in the VHDL description

```

library ieee;
use ieee.std_logic_1164.all;

entity Rot_shifter is port(s :in bit_vector(0 to 2);
    i :in bit_vector(0 to 7);
    o :out bit_vector(0 to 7));
end Barrel_shifter;

architecture demo of Rot_shifter is
begin process (s, i)
begin
    case s is
        WHEN "000"=>
            o<=i;
        WHEN "001"=>
            o<=(i(1),i(2),i(3),i(4),i(5),i(6),i(7),i(0));
        WHEN "010"=>
            o<=(i(2),i(3),i(4),i(5),i(6),i(7),i(0),i(1));
        WHEN "011"=>
            o<=(i(3),i(4),i(5),i(6),i(7),i(0),i(1),i(2));
        WHEN "100"=>
            o<=(i(4),i(5),i(6),i(7),i(0),i(1),i(2),i(3));
        WHEN "101"=>
            o<=(i(5),i(6),i(7),i(0),i(1),i(2),i(3),i(4));
        WHEN "110"=>
            o<=(i(6),i(7),i(0),i(1),i(2),i(3),i(4),i(5));
        WHEN "111"=>
            o<=(i(7),i(0),i(1),i(2),i(3),i(4),i(5),i(6));
    end case;
end process;
    
```

 

Simulation results in ACTIVE-Sim

S	O
000	10000000
001	00000001
010	00000010
011	00000100
100	00001000
101	00010000
110	00100000
111	01000000

Simulation results in a table

VHDL description of 8-bit rotation with CASE