 


Пример 5. 4-битов суматор описан на VHDL със структурен модел

1. Логическа схема на 4-битов суматор:



Фиг.1. 4-битов суматор - A_0 е младшият бит, A_3 е старшият бит

2. Принцип на действие:

4-битовият суматор е логическа схема, която изчислява сумата на две 4-битови двоични числа.

Проектираният суматор е с последователен пренос. Той се състои от 4 последователно свързани еднобитови суматори. Първият пълен суматор е отговорен за събирането на първите две цифри на 4-битовото число, вторият за събирането на вторите две цифри, като към тях прибавя и остатъка от предния суматор и така, докато всичките битове на числото бъдат събрани.

3. Логически уравнения:

Входове: $A=A_3A_2A_1A_0$ Изходи: $S=S_3S_2S_1S_0$
 $B=B_3B_2B_1B_0$ $C_{OUT}=C_4$
 $C_{in}=C_0$

$S_0 = (A_0 \text{ XOR } B_0) \text{ XOR } C_0;$

$C_1 = (A_0 \text{ AND } B_0) \text{ OR } (C_0 \text{ AND } B_0) \text{ OR } (C_0 \text{ AND } A_0)$

$S_1 = (A_1 \text{ XOR } B_1) \text{ XOR } C_1;$

$C_2 = (A_1 \text{ AND } B_1) \text{ OR } (C_1 \text{ AND } B_1) \text{ OR } (C_1 \text{ AND } A_1)$

$S_2 = (A_2 \text{ XOR } B_2) \text{ XOR } C_2;$

$C_3 = (A_2 \text{ AND } B_2) \text{ OR } (C_2 \text{ AND } B_2) \text{ OR } (C_2 \text{ AND } A_2)$

$S_3 = (A_3 \text{ XOR } B_3) \text{ XOR } C_3;$

$C_4 = (A_3 \text{ AND } B_3) \text{ OR } (C_3 \text{ AND } B_3) \text{ OR } (C_3 \text{ AND } A_3)$

4. Описание на 4-битов суматор на VHDL със структурен модел, който използва като компонент еднобитов суматор:


```
library ieee;
use ieee.std_logic_1164.all;
entity adder_1_bit is port (a,b,Cin : in std_logic; S, Cout : out std_logic);
end adder_1_bit;
architecture structure of adder_1_bit is
begin
    process (a,b,Cin)
    begin
        S<= a xor b xor Cin;
        Cout<= (a and b) or (b and Cin) or (a and Cin);
    end process;
end structure;
library ieee;
use ieee.std_logic_1164.all;
entity adder_4_bit is
    port ( Cin: in std_logic;
          a,b: in std_logic_vector(3 downto 0);
          S: out std_logic_vector(3 downto 0);
          Cout: out std_logic );
end adder_4_bit;
architecture structure of adder_4_bit is
    signal t: std_logic_vector (4 downto 0);
    constant n: integer:=4;
begin
    t(0) <=Cin; Cout <=t(n);
    FA_f: for i in 0 to n-1 generate
        FA_i: adder_1_bit port map (t(i), a(i), b(i), S(i), t(i+1));
    end generate;
end structure;
```

Пример 5. 4-битов суматор – описан на VHDL със структурирен модел
 Автори: Силвия Петрова, Галя Маринова, 01.02.2010 г.

5. Входни сигнали:

| Signal | Type | Frequency |
|--------|----------|---|
| A | Constant | 0 |
| b | Formulae | 0.4 us 0 0.8 us 1 1.2 us 2 1.6 us 3 2 us 4 2.4 us 5 |
| Cin | Clock | 10Mhz |

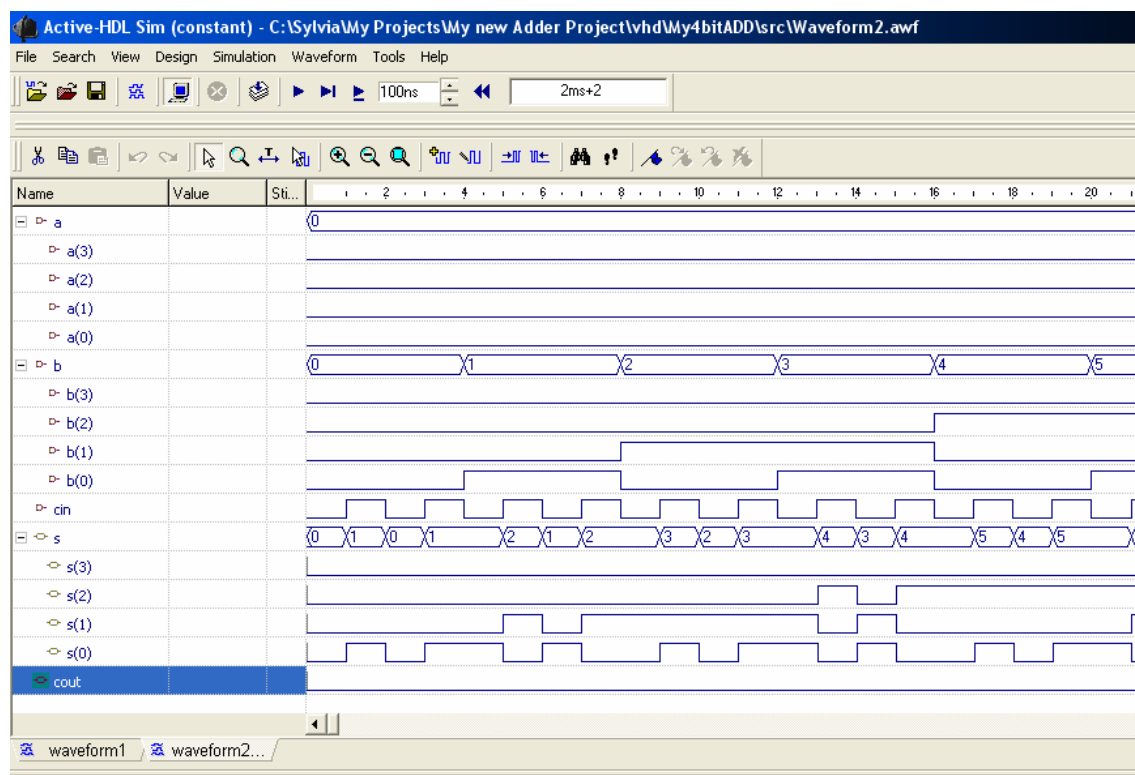6. Резултати от симулацията в ACTIVE-HDL SIM:



Входните и изходните сигнали са представени като 4-битови магистрали и като десетични числа.

7. Използвани ресурси върху програмируемата схема CY37256P160-83AC и закъснения от REPORT файла adder_4_bit.rpt:

RESOURCE UTILIZATION (15:08:01)

Information: Macrocell Utilization.

| Description | Used | Max |
|-------------------|------|-----|
| Dedicated Inputs | 1 | 1 |
| Clock/Inputs | 4 | 4 |
| I/O Macrocells | 13 | 128 |
| Buried Macrocells | 3 | 128 |

Пример 5. 4-битов суматор – описан на VHDL със структурирен модел
Автори: Силвия Петрова, Галя Маринова, 01.02.2010 г.

| PIM Input Connects | 23 | 624 |

44 / 885 = 4 %

| | Required | Max (Available) |
|----------------------------|----------|-----------------|
| CLOCK/LATCH ENABLE signals | 0 | 20 |
| Input REG/LATCH signals | 0 | 133 |
| Input PIN signals | 5 | 5 |
| Input PINs using I/O cells | 4 | 4 |
| Output PIN signals | 5 | 124 |

| | Required | Max (Available) |
|----------------------|----------|-----------------|
| Total PIN signals | 14 | 133 |
| Macrocells Used | 12 | 256 |
| Unique Product Terms | 107 | 1280 |

TIMING PATH ANALYSIS (15:08:02) using Package: cy37256p160-83ac

Messages:

Signal Name | Delay Type | tmax | Path Description

cmb::s(0)[42]
inp::b(0)

tPD 15.0 ns 1 pass

cmb::s(1)[52]
inp::b(0)

tPD 15.0 ns 1 pass

cmb::s(3)[63]
inp::b(0)

---->S_1

tPD 26.0 ns 2 passes

cmb::s(2)[82]
inp::b(0)

---->S_4

tPD 26.0 ns 2 passes

cmb::cout[91]
inp::b(0)

---->S_6

tPD 26.0 ns 2 passes

Worst Case Path Summary

tPD = 26.0 ns for s(3)